 


《Digital Circuits and Logic Design》期末试题 (A 卷)


参考答案

1. Multiple choice questions (2 points for each question, 20 points total).


- (1) If the period of a clock signal is 500 ps, the frequency is c
- a. 20 MHz
 - b. 200 MHz
 - c. 2 GHz
 - d. 20 GHz
- (2) The time measurement between the 90% point on the trailing edge of a pulse to the 10% point on the trailing edge of the pulse is called the b
- a. rise time
 - b. fall time
 - c. period
 - d. pulse width
- (3) When two positive signed numbers are added, the result may be larger than the size of the original numbers, creating overflow. This condition is indicated by a
- a. a change in the sign bit
 - b. a carry out of the sign position
 - c. a zero result
 - d. smoke
- (4) Assume that a floating point number is represented in binary. If the sign bit is 1, the a
- a. number is negative
 - b. number is positive
 - c. exponent is negative
 - d. exponent is positive
- (5) A Boolean expression that is in standard SOP form is c
- a. the minimum logic expression
 - b. contains only one product term
 - c. has every variable in the domain in every term
 - d. none of the above
- (6) The time interval illustrated is called b
- a. t_{PHL}
 - b. t_{PLH}
 - c. set-up time
 - d. hold time



 
- (7) The application illustrated is a d
- a. astable multivibrator
 - b. data storage device
 - c. frequency multiplier
 - d. frequency divider



 - (8) Assume you want to decode the binary number 0011 with an active-HIGH decoder. The missing gate should be d
- a. an AND gate
 - b. an OR gate
 - c. a NAND gate
 - d. a NOR gate




 - (9) If the data select lines of the MUX are $S_1S_0 = 11$, the output will be d
- a. LOW
 - b. HIGH
 - c. equal to D_0
 - d. equal to D_3



(10) Assume Q_0 is LOW. The next clock pulse will cause **b**

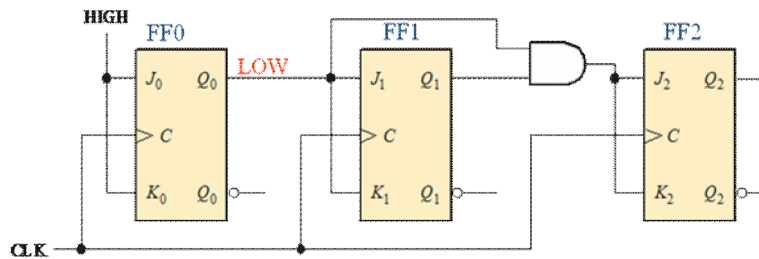- a. FF1 and FF2 to both toggle
- b. FF1 and FF2 to both latch
- c. FF1 to latch; FF2 to toggle
- d. FF1 to toggle; FF2 to latch



© 2008 Pearson Education

2. Please solve the following number conversion problems (total 15 points)

- (1) Convert binary number 10111000.10101 to decimal (2 points)
- (2) Convert decimal number 100.625 to binary (2 points)
- (3) Express decimal number -85 as 8-bit number in 1's complement form (2 points)
- (4) Express decimal number -85 as 8-bit number in 2's complement form (2 points)
- (5) Convert decimal number 126 to (3 points)
 - (a) Hexadecimal number
 - (b) Octal number
 - (c) 8421 BCD number
- (6) Convert the decimal number 3.248×10^4 to a single-precision floating point binary number. Please show your procedure (4 points)

-
- (1) 184.65625
 - (2) 110 0100.101
 - (3) 1010 1010
 - (4) 1010 1011
 - (5) (a) H7E (b) O176 (c) 0001 0010 0110
 - (6) 0 10001101 111_1101_1100_0000_0000_0000

-
3. We need to design a circuit with 4 inputs(marked as A, B,C,D) and 2 outputs X, Y. Based on system analysis, we should have true table as shown in the following (total 20 points):

| A | B | C | D | X | Y |
|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 1 | 0 |
| 0 | 0 | 1 | 0 | 1 | 1 |
| 0 | 0 | 1 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 | 1 |

- (1) Express the above circuit's outputs in minimum Sum-of-Product (SOP) form (4 points)
- (2) Show the implementation of the circuit in SOP form by using only AND, OR, or NOT gates (3 points)
- (3) Show the implementation of the circuit in SOP form by using only NAND gates (3 points)
- (4) Express the above circuit's outputs in minimum Product-of-Sum (POS) form (4 points)
- (5) Show the implementation of the circuit in POS form by using only AND, OR, or NOT gates (3 points)
- (6) Show the implementation of the circuit in POS form by using only NOR gates (3 points)

(1)

$$X = \overline{A}\overline{C}\overline{D} + \overline{B}\overline{C}\overline{D} + ABC\overline{D}$$

$$Y = \overline{A}D + \overline{B}\overline{C}D$$

(2)

$$X = \overline{A}\overline{C}\overline{D} + \overline{B}\overline{C}\overline{D} + ABC\overline{D}$$

The diagram is omitted.

$$Y = \overline{A}D + \overline{B}\overline{C}D$$

(3)

$$X = \overline{\overline{\overline{A}\overline{C}\overline{D}} \bullet \overline{\overline{\overline{B}\overline{C}\overline{D}}} \bullet \overline{\overline{\overline{ABC\overline{D}}}}}$$

The diagram is omitted.

$$Y = \overline{\overline{\overline{A}D} \bullet \overline{\overline{\overline{B}\overline{C}D}}}$$

(4)

$$X = (A + C + D)(B + C + D)(\bar{A} + \bar{B} + \bar{C} + D)$$

$$Y = (A + \bar{D})(B + C + \bar{D})$$

(5)

$$X = (A + C + D)(B + C + D)(\bar{A} + \bar{B} + \bar{C} + D)$$

The diagram is omitted.

$$Y = (A + \bar{D})(B + C + \bar{D})$$


(6)

$$X = \overline{\overline{A + C + D} + \overline{B + C + D} + \overline{\bar{A} + \bar{B} + \bar{C} + D}}$$

The diagram is omitted.

$$Y = \overline{\overline{A + \bar{D}} + \overline{B + C + \bar{D}}}$$

 4. Design a 2-bit look-ahead-carry full adder using only basic logic gates (AND, OR, NOT, NAND, NOR, XOR, XNOR). (total 15 points)



$$\text{Denote } C_{out1} = A_1 B_1 + (A_1 + B_1) C_{in}$$

$$\Sigma_1 = A_1 \oplus B_1 \oplus C_{in}$$

$$\Sigma_2 = A_2 \oplus B_2 \oplus C_{in1}$$

$$C_{out} = A_2 B_2 + (A_2 + B_2) C_{in1}$$

5. Design a Moore FSM to detect a bit sequence 11001. If such sequence is found, output will be set to 1, otherwise, output will be set to 0. Overlap sequence, if exists, should be detected. Please use J-K flip flop for the system. (total 30 points).

- (1) Derive state diagram (4 points)
- (2) Encode states (state assignment) (2 points)
- (3) Create state-assigned state table (4 points)
- (4) Express J-K Flip-Flop excite table to use (3 points)
- (5) Determine minimum Flip-Flop input equations and FSM output equation(s) (8 points)
- (6) Verify that there is no state that will stay outside the FSM for ever (2 points)
- (7) Draw circuit diagram (7 points)

Keypoints.

-- 'S0' indicates no '1's has been input yet. So the output at this state is '0'.

S1: only one '1' has been input; output '0'.


S2: input '11'; output '0'.

S3: input '110'; output '0'.

S4: input '1100'; output '0'.

S5: input '11001'; output '1'.

 -- Denote X as the input and Y the output. The state diagram is shown as follow.



-- Three JK Flip-flops are used in this design. The outputs of JK Flip-flops will indicate the states shown in the above diagram.

-- '000' – 'S0'; '001' – 'S1'; '010' – 'S2'; '011' – 'S3'; '100' – 'S4'; '101' – 'S5'. Others are inactive states. Incorporating this state-assignment, the state diagram above can be translated into the Next-State Karnaugh Map.

| Q ₂ Q ₁ \ Q ₀ X | 00 | 01 | 11 | 10 |
|--------------------------------------------------|-------|-------|-------|-------|
| 00 | 000/0 | 001/0 | 010/0 | 000/0 |
| 01 | 010/0 | 011/0 | 001/0 | 100/0 |
| 11 | 000/0 | 101/1 | 000/0 | 010/0 |
| 10 | XXX/X | XXX/X | XXX/X | XXX/X |

--

$$Q_2^{n+1} = Q_2^n \overline{Q_0^n} X + \overline{Q_2^n} Q_1^n Q_0^n \overline{X}$$

$$Q_1^{n+1} = \overline{Q_2^n} Q_1^n \overline{Q_0^n} + \overline{Q_1^n} Q_0^n X + Q_2^n Q_0^n \overline{X}$$

$$Q_0^{n+1} = \overline{Q_0^n} X + \overline{Q_2^n} Q_1^n X$$

$$Y = Q_2^n \overline{Q_0^n} X$$

--

$$\begin{aligned}
 J_2 &= Q_1^n Q_0^n \overline{X} & K_2 &= \overline{\overline{Q_0^n X}} \\
 J_1 &= Q_0^n X + Q_2^n Q_0^n \overline{X} & K_1 &= \overline{\overline{Q_2^n Q_0^n} + Q_2^n Q_0^n \overline{X}} \\
 J_0 &= X & K_0 &= \overline{\overline{Q_2^n Q_1^n X}}
 \end{aligned}$$

- The circuit design is capable of booting itself.
- The logic diagram is omitted.